

FPGA Lab Assignment 1

EE20MTECH14016 - Pulkit Saxena

1 QUESTION

[CBSE 2019 Q6 (a)] State any one Distributive Law of Boolean Algebra and verify it using truth table.

2 SOLUTION

Distributive Law is as follows:-

$$A.(B + C) \quad (2.1)$$

$$= A.B + A.C \quad (2.2)$$

3 TRUTH TABLE

Verification of the above stated distributive law using truth table is as follows.

A	B	C	B+C	A.(B+C)	A.B	A.C	A.B+A.C
0	0	0	0	0	0	0	0
0	0	1	1	0	0	0	0
0	1	0	1	0	0	0	0
0	1	1	1	0	0	0	0
1	0	0	0	0	0	0	0
1	0	1	1	1	0	1	1
1	1	0	1	1	1	0	1
1	1	1	1	1	1	1	1


$$A.(B + C) = A.B + A.C \quad (3.1)$$

4 KARNAUGH MAP

A \ BC	BC			
	00	01	11	10
0	0	0	0	0
1	0	1	1	1

Fig. 1: K-Map for $A.B + A.C$

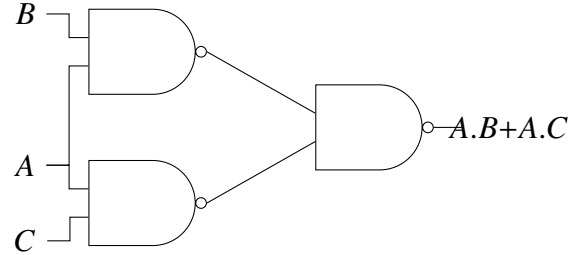5 CIRCUIT DIAGRAM(IMPLEMENTATION USING NAND GATES)



Proof:-

$$\overline{\overline{A.B.A.C}} = \overline{\overline{A.B}} + \overline{\overline{A.C}} \quad (5.1)$$

$$\Rightarrow A.B + A.C \quad (5.2)$$

The eq 5.1 is through Demorgan's law.